



GS-379

IV Semester B.Sc. Examination, May/June - 2019

ELECTRONICS - IV

Digital Electronics and Verilog
(CBCS)(F+R) (2015-16 & Onwards)



Time : 3 Hours

Max. Marks : 70

- Instructions :** (1) Answer **all** questions from **Part-A**, **any five** questions from **Part-B** and **any four** questions from **Part-C**.
- (2) It is required to answer **all** questions of **Part-A** in **any one** page and to be answered only once. In this Part answering the same question multiple times will not be considered for evaluation.

PART - A

1. Answer **all** the subdivisions :

15x1=15

- (i) A quantity having continuous values is :
 - (a) digital
 - (b) analog
 - (c) a binary
 - (d) all the above
- (ii) The output of an AND gate is HIGH when :
 - (a) any input is HIGH
 - (b) all inputs are HIGH
 - (c) None of the inputs are HIGH
 - (d) both (a) and (b)
- (iii) In a certain digital circuit, the time period of the applied signal is twice the pulse width. The duty cycle is :
 - (a) 100%
 - (b) 200%
 - (c) 50%
 - (d) 66.66%
- (iv) A4-variable Karnaugh Map has :
 - (a) three cells
 - (b) eight cells
 - (c) sixteen cells
 - (d) four cells
- (v) Block Diagram of half-adder consists of :
 - (a) two inputs and two outputs
 - (b) three inputs and two outputs
 - (c) two inputs and three outputs
 - (d) two inputs and one output
- (vi) In a 4-bit binary weighted resistor type D/A converter most significant bit resistor is 10 k Ω . The least significant bit resistor used is :
 - (a) 1.25 k Ω
 - (b) 12.5 k Ω
 - (c) 40 k Ω
 - (d) 80 k Ω
- (vii) A JK flip-flop is in toggle state when :
 - (a) J=1, K=0
 - (b) J=1, K=1
 - (c) J=0, K=0
 - (d) J=0, K=1
- (viii) The content of a 4-bit register is 1001. The register is shifted 3 times to the left. The content of the register will be :
 - (a) 1000
 - (b) 0011
 - (c) 0110
 - (d) 1001

P.T.O.




- (ix) Register is a :
 (a) Set of instructions in a digital computer
 (b) Set of paper tapes and cards put in a file
 (c) Sequential circuit
 (d) None of the above
- (x) In order to build a mod-14 down counter the minimum number of flip flops required are :
 (a) 5 (b) 2 (c) 4 (d) 3
- (xi) Which module is available in Verilog but not in VHDL ?
 (a) Behavioral level (b) Switch level
 (c) Gate level (d) Data flow level
- (xii) Which logic level is **not** supported by Verilog ?
 (a) F (b) X (c) Z (d) 1
- (xiii) In Verilog the identifier beginning with _____ character is interpreted as a system task or as system function.
 (a) # (b) // (c) \$ (d) ^
- (xiv) In Verilog 'h2A3' is a :
 (a) 16-bit Hex number (b) 32-bit Hex number
 (c) 4-bit Hex number (d) 8-bit Hex number
- (xv) If time scale is defined as timescale 10ns/1ns and #1.75 a=b; then 'a' gets 'b' after
 (a) 10 ns (b) 11 ns (c) 17.5 ns (d) 18 ns

PART - B

Answer **any five** questions.

5x7=35

 
2. Verify the universal property of NOR gate by realizing AND, OR, NAND and XNOR gates. 7
3. (a) What is Full-adder ? Draw the circuit diagram using logic gates and write its truth table. 4
 (b) What is a demultiplexer ? Draw the logic diagram of 1 : 4 demultiplexer. 3
4. (a) With a circuit diagram, explain the working of 4-bit binary weighted D to A converter. 5
 (b) Differentiate between combinational and sequential logic circuits. 2
5. Explain the working of clocked RS flip-flop with circuit diagram using only NAND gate. Draw the truth table and timing diagram. 7
6. What is a shift register ? Draw the logic diagram of a 4-bit serial-in serial-out shift register. Explain how the data 1010 is written and retrieved. Also draw the timing diagram. 7



7. (a) Compare VHDL and Verilog. 5+2
(b) Write the basic module of Verilog Programming.
8. Explain Logical and Reduction operators in Verilog with examples. 7
9. Explain initial and always statements in behavioral modeling. 7

PART - CAnswer **any four** questions.**4x5=20**

 10. Write the Boolean expression for the output Y in the given logic diagram by mentioning the output at the end of each gate and simplify it using Boolean Laws. 5



11. Simplify the Boolean function $f(A, B, C, D) = \sum m(1, 3, 5, 8, 9, 11, 15) + \sum d(0, 2, 13)$ Using K-map and realize the simplified expression using basic gates. 5
12. A 4-bit Digital to Analog Converter has a step size of 0.20 V. Determine output voltage for input of 1101 if reference voltage is 5 V and also calculate percentage of resolution. 5
13. Design a synchronous mod-3 counter using K-map technique. 5
14. Write a Verilog code for binary to gray code and vice-versa. 5
15. Write a Verilog code for 4 : 1 Multiplexer. 5